


Ecuaciones principales

- $V_c(t) = R i_1(t) + \frac{L d[i_1(t) - i_2(t)]}{dt} + R [i_1(t) - i_2(t)]$
- $\frac{L d[i_1(t) - i_2(t)]}{dt} + R [i_1(t) - i_2(t)] = R i_2(t) + R i_2(t) + \frac{1}{C} \int i_2(t) dt$
- $V_s(t) = R i_2(t) + \frac{1}{C} \int i_2(t) dt$

Modelo de

Ecuaciones integro-diferenciales

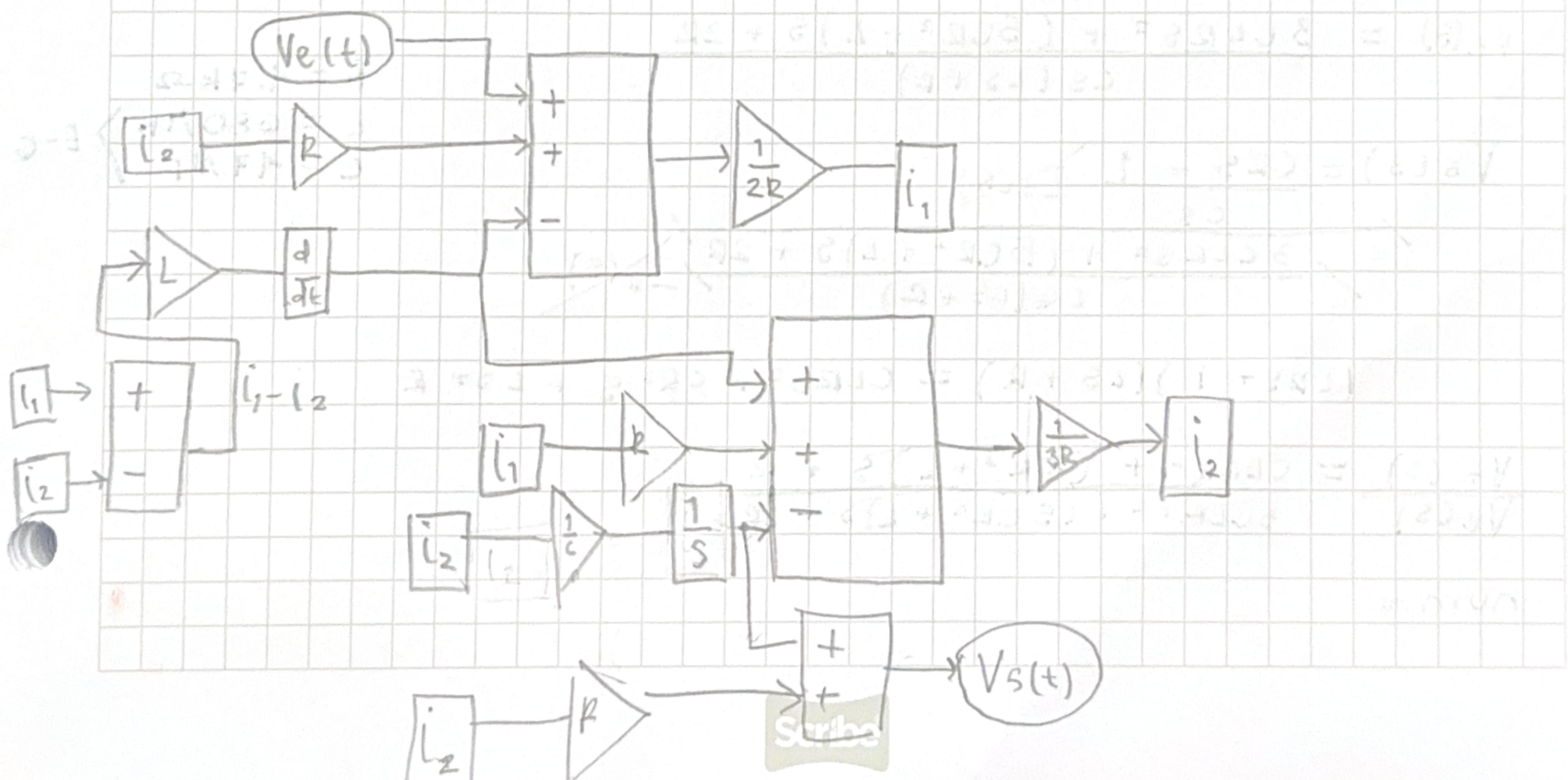- $i_1(t) = \left[ V_c(t) - \frac{L d[i_1(t) - i_2(t)]}{dt} + R i_2(t) \right] \frac{1}{2R}$
- $i_2(t) = \left[ \frac{L d[i_1(t) - i_2(t)]}{dt} + R i_1(t) - \frac{1}{C} \int i_2(t) dt \right] \frac{1}{3R}$
- $V_s(t) = R i_2(t) + \frac{1}{C} \int i_2(t) dt$



• Transformada de Laplace

$$V_e(s) = RI_1(s) + LS[I_1(s) - I_2(s)] + R[I_1(s) - I_2(s)]$$

$$LS[I_1(s) - I_2(s)] + R[I_1(s) - I_2(s)] = RI_2(s) + RI_1(s) + \frac{I_2(s)}{CS}$$

$$V_s(s) = RI_2(s) + \frac{I_2(s)}{CS}$$

• Procedimiento algebraico

$$V_e(s) = (R + LS + R)I_1(s) - (LS + R)I_2(s)$$

$$= (LS + 2R)I_1(s) - (LS + R)I_2(s)$$

$$LSI_1(s) - LSI_2(s) + RI_1(s) - RI_2(s) = 2RI_2(s) + \frac{I_2(s)}{CS}$$

$$LSI_1(s) + RI_1(s) = 3RI_2(s) + LSI_2(s) + \frac{I_2(s)}{CS}$$

$$(LSI_1(s) + RI_1(s)) = \left(3R + LS + \frac{1}{CS}\right)I_2(s)$$

$$I_1(s) = \frac{3CRS + CLS^2 + 1}{CS(LS+R)} I_2(s) = \frac{CLS + 3CRS + 1}{CS(LS+R)} I_2(s)$$

$$V_e(s) = \frac{(LS + 2R)(CLS^2 + 3CRS + 1)}{CS(LS+R)} I_2(s) - (LS + R)I_2(s)$$

$$= \left[ \frac{(LS + 2R)(CLS^2 + 3CRS + 1)}{CS(LS+R)} - \frac{CS(LS+R)(LS+R)}{5CR^2S} \right] I_2(s)$$

$$\cancel{CL^2S^3} + 3CLR^2S^2 + LS + 2\cancel{CLRS^2} + \cancel{6CR^2S} + 2R - \cancel{CL^2S^3} - \cancel{2CLRS^2} - \cancel{CR^2S}$$

$$V_e(s) = \frac{3CLR^2S^2 + (5CR^2 + L)S + 2R}{CS(LS+R)}$$

$$R = 4.7k\Omega$$

$$L = 680\text{mH}$$

$$C = 17\text{nF} \quad E-6$$

$$V_s(s) = \frac{CRS + 1}{CS} \cancel{I_2(s)}$$

$$\frac{3CLR^2S^2 + (5CR^2 + L)S + 2R}{CS(LS+R)} \cancel{I_2(s)}$$

$$(CRS + 1)(LS + R) = CLR^2S^2 + CR^2S + LS + R$$

$$\frac{V_s(s)}{V_e(s)} = \frac{CLR^2S^2 + (CR^2 + L)S + R}{3CLR^2S^2 + (5CR^2 + L)S + 2R}$$

$$\text{num} =$$

- Estabilidad en lazo abierto

- calcular los polos de la función de transferencia

$$\frac{V_s(s)}{V_e(s)} = \frac{CLRS^2 + (CR^2 + L)s + R}{3CLRS^2 + (5CR^2 + L)s + 2R}$$

$$\text{den} = [3 \times C \times L \times R, 5 \times C \times R^2 + 2 + L, 2 \times R]$$

$$L = n^2$$

- Error en estado estacionario

$$e(s) = \lim_{s \rightarrow 0} s V_e(s) \left[ 1 - \frac{V_s(s)}{V_e(s)} \right] \quad V_e(t) = 1 \quad V_e(s) = \frac{1}{s}$$

$$= \lim_{s \rightarrow 0} s \times \frac{1}{s} \left[ 1 - \frac{CLRS^2 + (CR^2 + L)s + R}{3CLRS^2 + (5CR^2 + L)s + 2R} \right]$$

$$= \frac{k}{2R}$$

El sistema presenta una respuesta estable y sobremortiguada

$$e(t) = \frac{1}{2}$$

